


Digital Design & Computer Architecture

Sarah Harris & David Harris

Chapter 7: Microarchitecture

Introduction

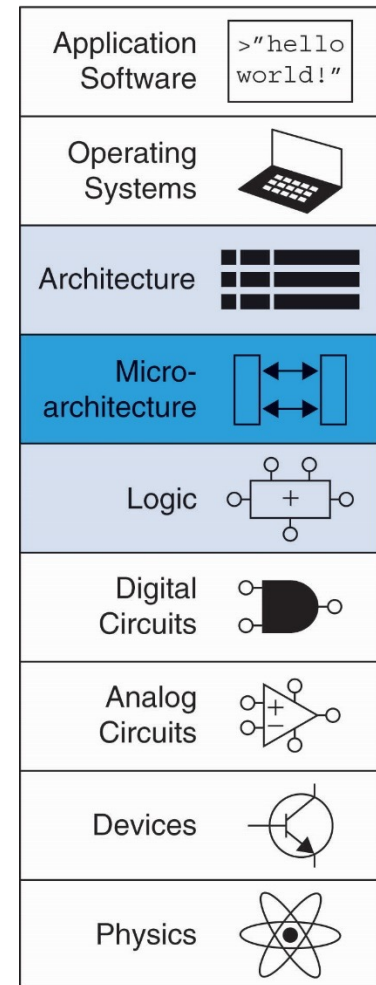
- **Microarchitecture:** how to implement an architecture in hardware
- Processor:
 - **Datapath:** functional blocks
 - **Control:** control signals



Microarchitecture

- **Multiple implementations** for a single architecture:
 - **Single-cycle:** Each instruction executes in a single cycle
 - **Multicycle:** Each instruction is broken up into series of shorter steps
 - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once

RISC-V Architectural State Elements

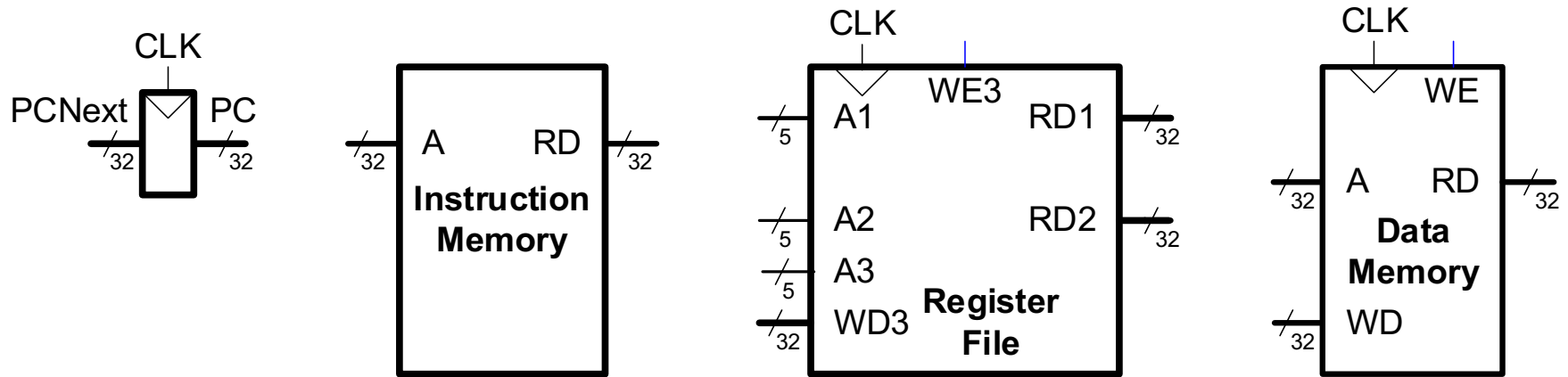

Example Program

- Design datapath
- View example program executing


Example Program:

Address	Instruction	Type	Fields					Machine Language	
0x1000	L7: lw x6, -4(x9)	I	imm _{11:0}	rs1	f3	rd	op		
			1111111111100	01001	010	00110	0000011	FFC4A303	
0x1004	sw x6, 8(x9)	S	imm _{11:5}	rs2	rs1	f3	imm _{4:0}	op	
			0000000 00110	01001	010	01000	0100011	0064A423	
0x1008	or x4, x5, x6	R	funct7	rs2	rs1	f3	rd	op	
			0000000 00110	00101	110	00100	0110011	0062E233	
0x100C	beq x4, x4, L7	B	imm _{12,10:5}	rs2	rs1	f3	imm _{4:1,11}	op	
			1111111 00100	00100	000	10101	1100011	FE420AE3	

Single-Cycle RISC-V Processor


- **Datapath:** start with `lw` instruction
- **Example:** `lw x6, -4(x9)`
`lw rd, imm(rs1)`

I-Type

 

Single-Cycle Datapath: lw fetch


STEP 1: Fetch instruction

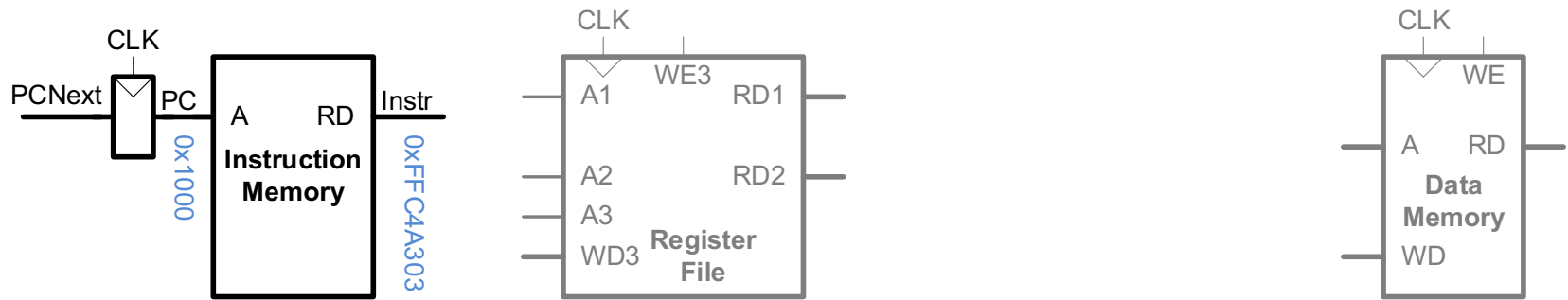

Address	Instruction	Type	Fields				Machine Language	
0x1000	L7: lw x6, -4(x9)	I	imm _{11:0}	rs1	f3	rd	op	
			1111111111100	01001	010	00110	0000011	FFC4A303

Single-Cycle Datapath: lw Reg Read

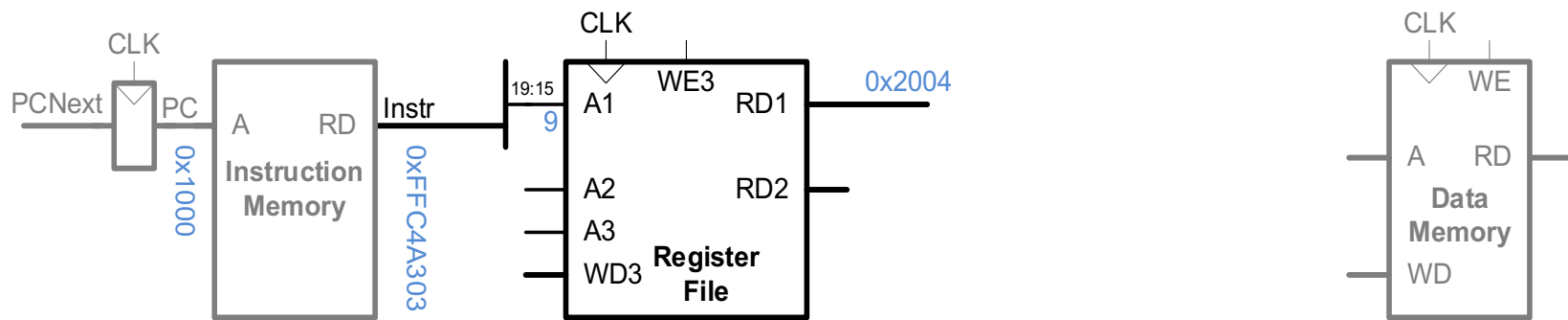
STEP 2: Read source operand (rs1) from RF



Address	Instruction	Type	Fields	Machine Language										
0x1000	L7: lw x6, -4(x9)	I	<table><tr><th>imm_{11:0}</th><th>rs1</th><th>f3</th><th>rd</th><th>op</th></tr><tr><td>1111111111100</td><td>01001</td><td>010</td><td>00110</td><td>0000011</td></tr></table>	imm _{11:0}	rs1	f3	rd	op	1111111111100	01001	010	00110	0000011	FFC4A303
imm _{11:0}	rs1	f3	rd	op										
1111111111100	01001	010	00110	0000011										

Single-Cycle Datapath: l_w Immediate


STEP 3: Extend the immediate

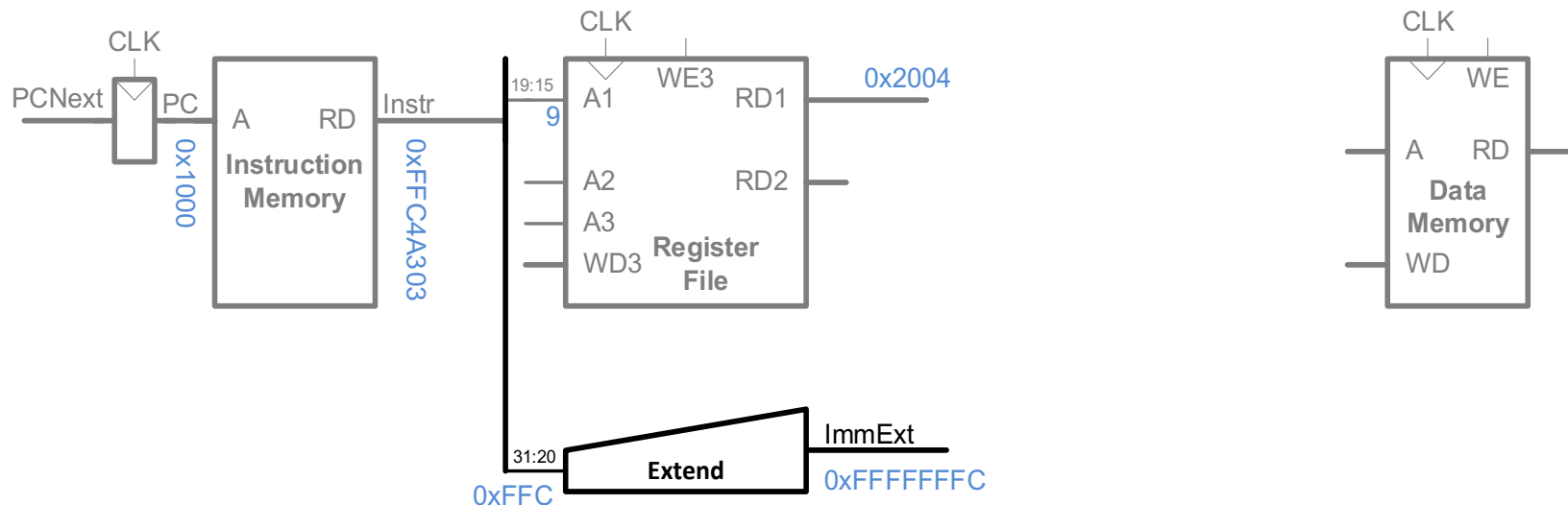

Address	Instruction	Type	Fields	Machine Language										
0x1000	L7: lw x6, -4(x9)	I	<table><tr><th>imm_{11:0}</th><th>rs1</th><th>f3</th><th>rd</th><th>op</th></tr><tr><td>1111111111100</td><td>01001</td><td>010</td><td>00110</td><td>0000011</td></tr></table>	imm _{11:0}	rs1	f3	rd	op	1111111111100	01001	010	00110	0000011	FFC4A303
imm _{11:0}	rs1	f3	rd	op										
1111111111100	01001	010	00110	0000011										

Single-Cycle Datapath: lw Address

STEP 4: Compute the memory address

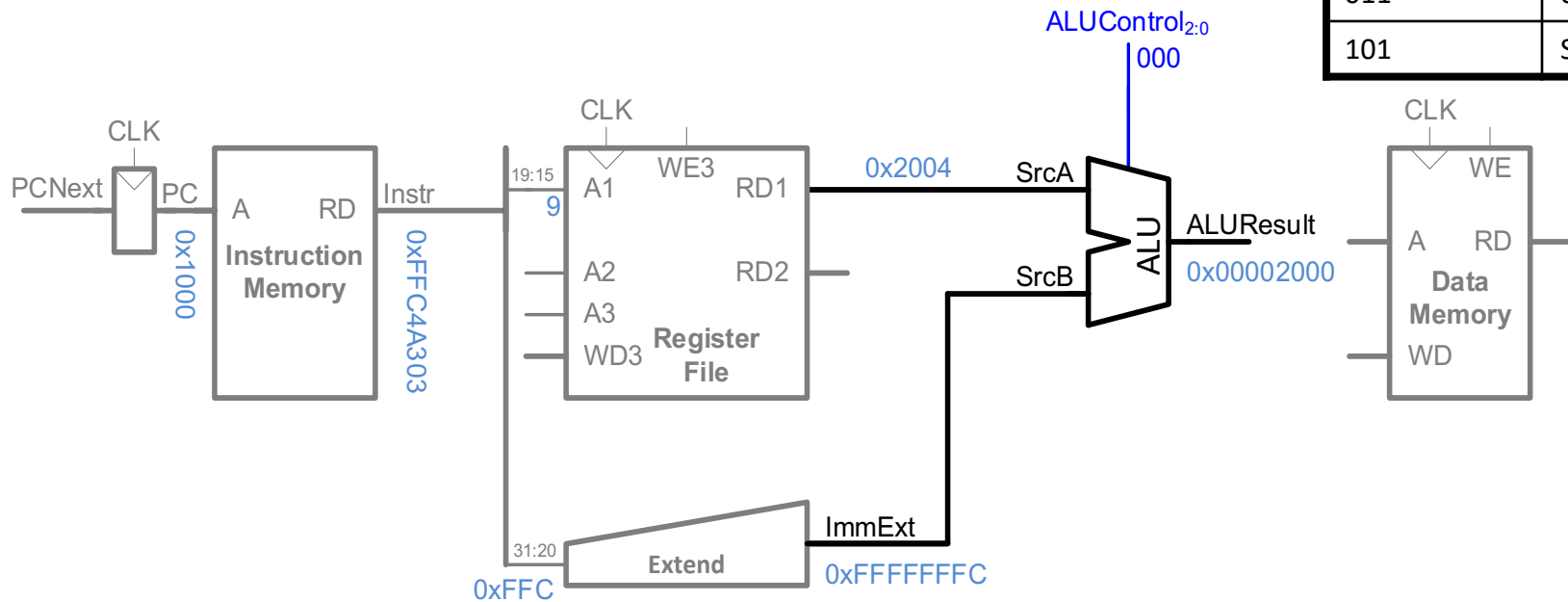


ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

Address	Instruction	Type	Fields				Machine Language	
0x1000	L7: lw x6, -4(x9)	I	imm _{11:0} 111111111100	rs1 01001	f3 010	rd 00110	op 0000011	FFC4A303

Single-Cycle Datapath: lw Mem Read

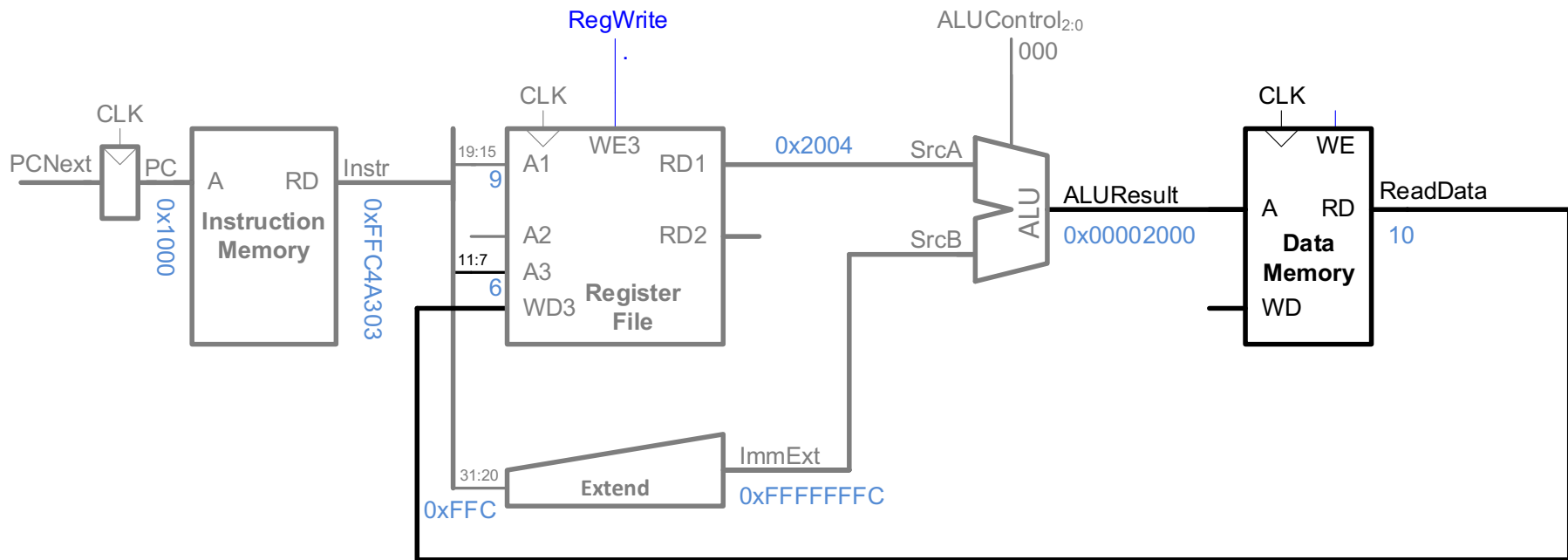
STEP 5: Read data from memory and write it back to register file



Address	Instruction	Type	Fields	Machine Language										
0x1000	L7: lw x6, -4(x9)	I	<table><tr><th>imm_{11:0}</th><th>rs1</th><th>f3</th><th>rd</th><th>op</th></tr><tr><td>1111111111100</td><td>01001</td><td>010</td><td>00110</td><td>0000011</td></tr></table>	imm _{11:0}	rs1	f3	rd	op	1111111111100	01001	010	00110	0000011	FFC4A303
imm _{11:0}	rs1	f3	rd	op										
1111111111100	01001	010	00110	0000011										

Single-Cycle Datapath: PC Increment

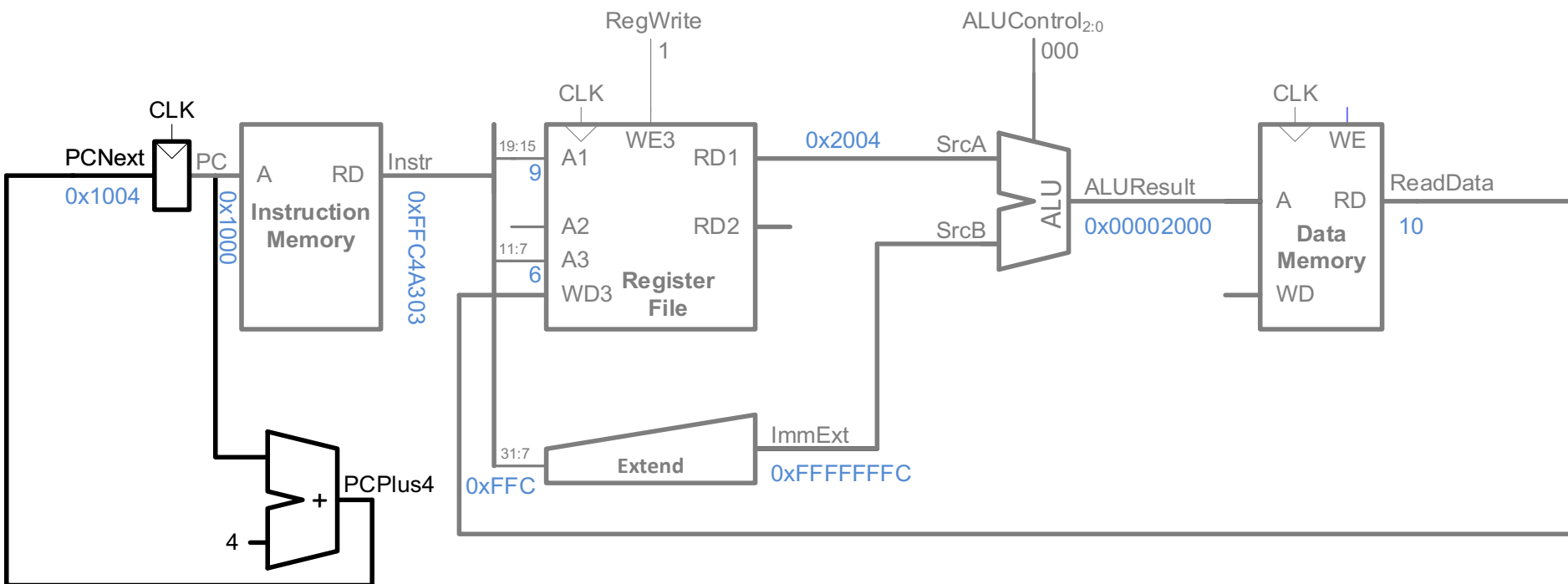STEP 6: Determine address of next instruction



Address	Instruction	Type	Fields			Machine Language	
			imm _{11:0}	rs1	f3	rd	op
0x1000	L7: lw x6, -4(x9)	I	111111111100	01001	010	00110	0000011
							FFC4A303


Chapter 7: Microarchitecture

Single-Cycle

**Datapath: Other
Instructions**

Single-Cycle Datapath: sw

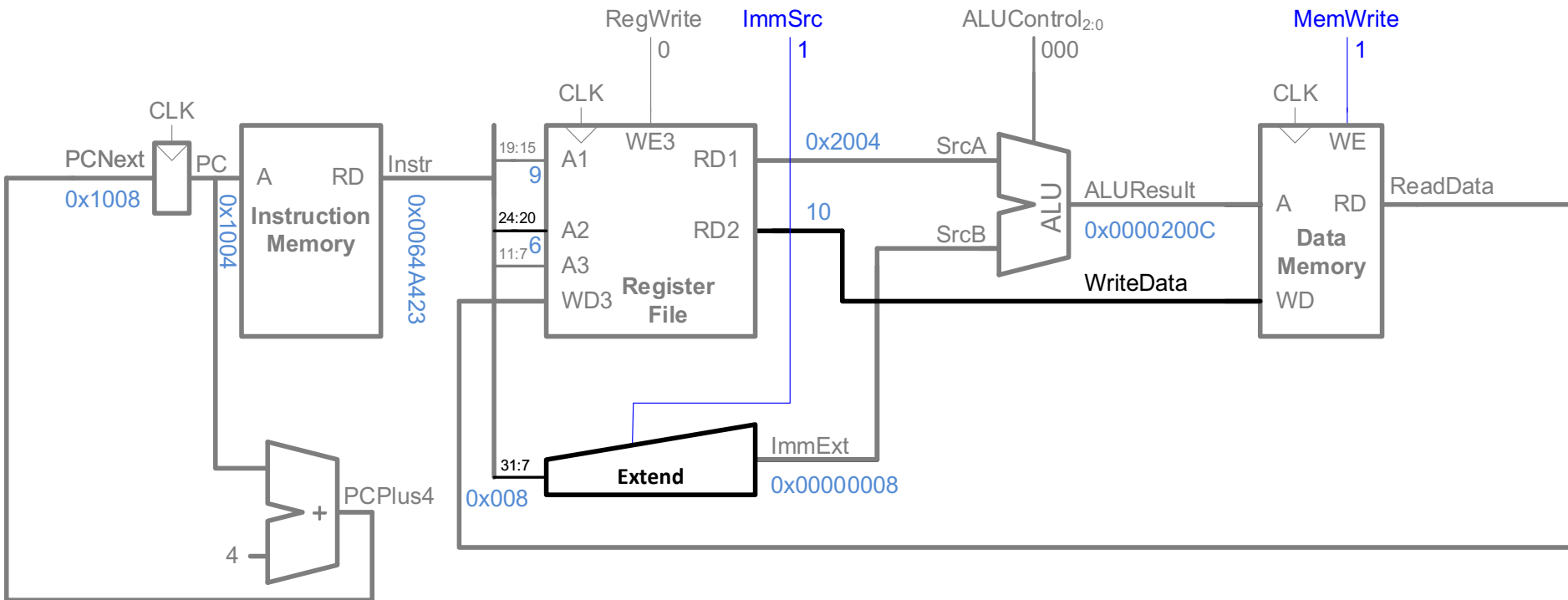
- **Immediate:** now in {instr[31:25], instr[11:7]}
- **Add control signals:** ImmSrc, MemWrite



Address	Instruction	Type	Fields	Machine Language
0x1004	sw x6, 8(x9)	S	imm _{11:5} 0000000 rs2 00110 rs1 01001 f3 010 imm _{4:0} 01000 op 0100011	0064A423

Single-Cycle Datapath: R-type

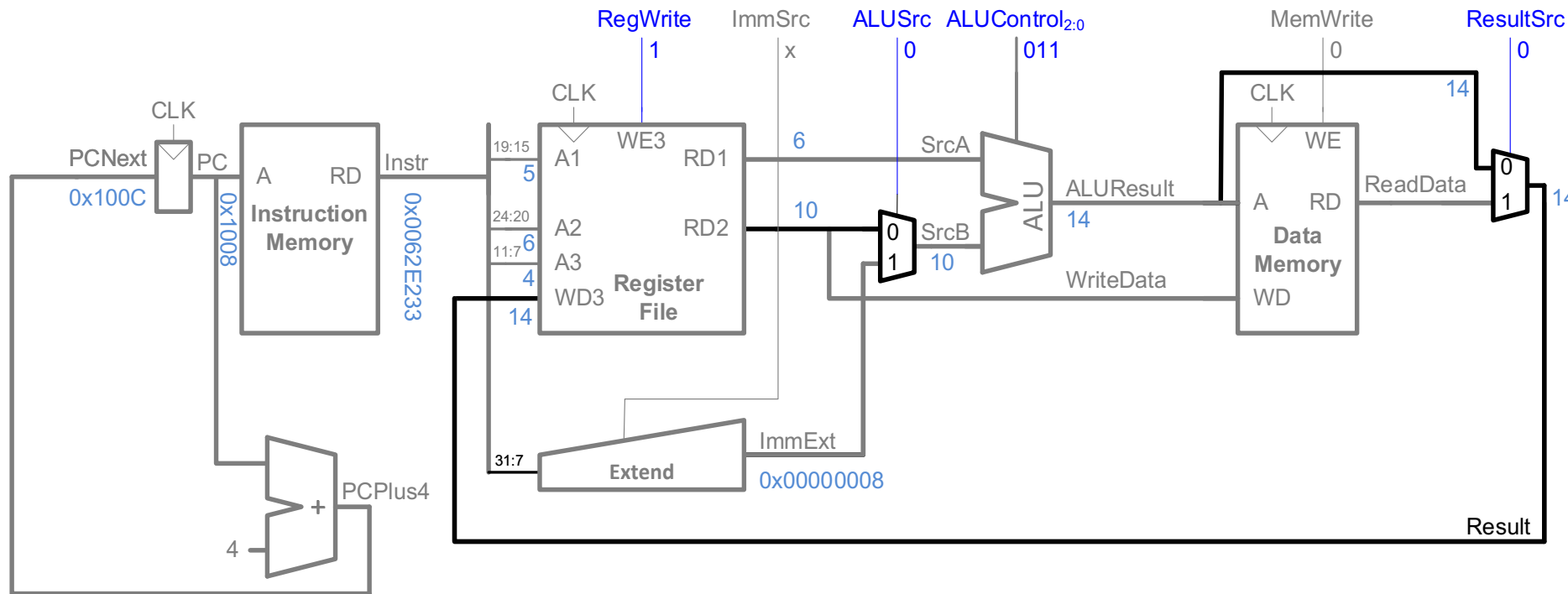
- Read from **rs1** and **rs2** (instead of **imm**)
- Write *ALUResult* to **rd**



Address	Instruction	Type	Fields					Machine Language	
0x1008	or x4, x5, x6	R	funct7	rs2	rs1	f3	rd	op	0062E233
			0000000	00110	00101	110	00100	0110011	

Single-Cycle Datapath: beq

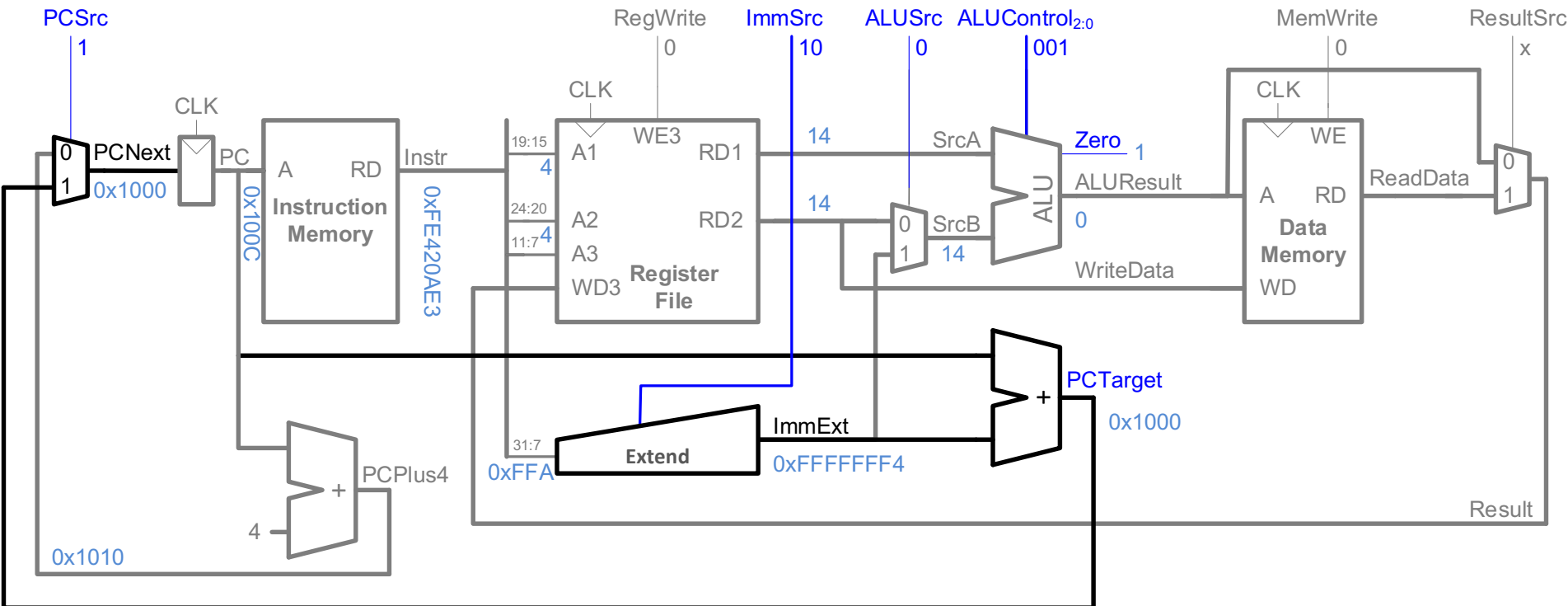Calculate **target address**: $PCTarget = PC + imm$




Address	Instruction	Type	Fields					Machine Language	
			$imm_{12,10:5}$	rs2	rs1	f3	$imm_{4:1,11}$	op	
0x100C	beq x4, x4, L7	B	1111111	00100	00100	000	10101	1100011	FE420AE3


Single-Cycle Datapath: ImmExt

ImmSrc _{1:0}	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20] }	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7] }	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0 }	B-Type


I-Type

 


S-Type

 

B-Type

 


Single-Cycle RISC-V Processor

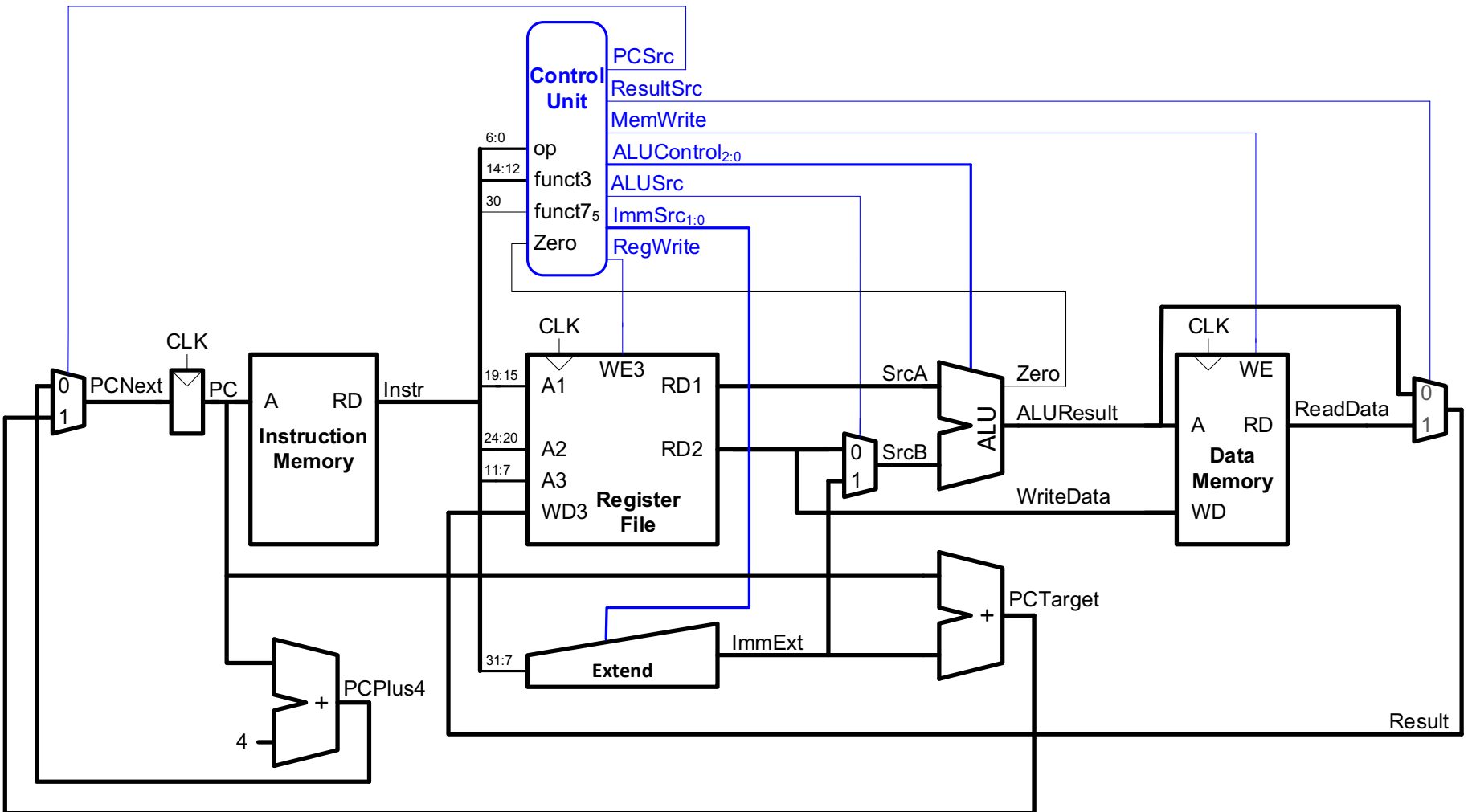


Single-Cycle Control

High-Level View

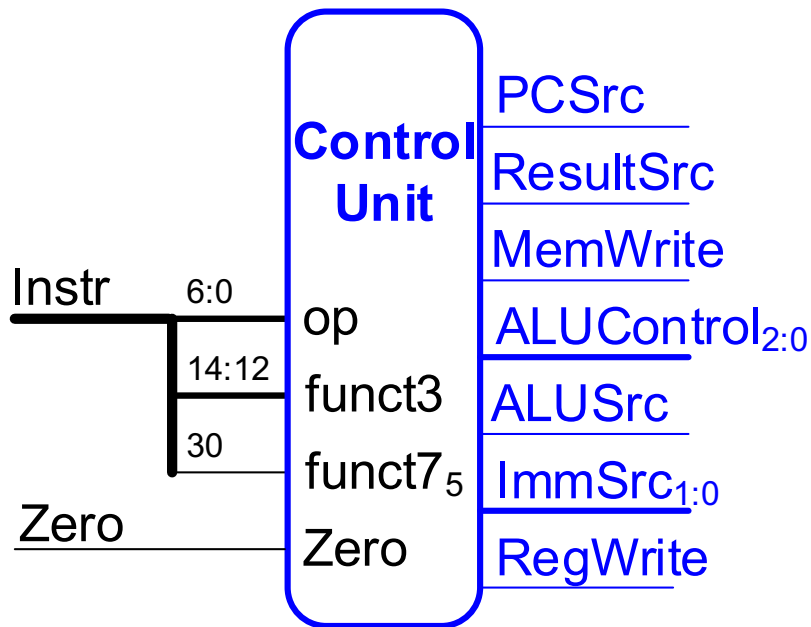


Low-Level View

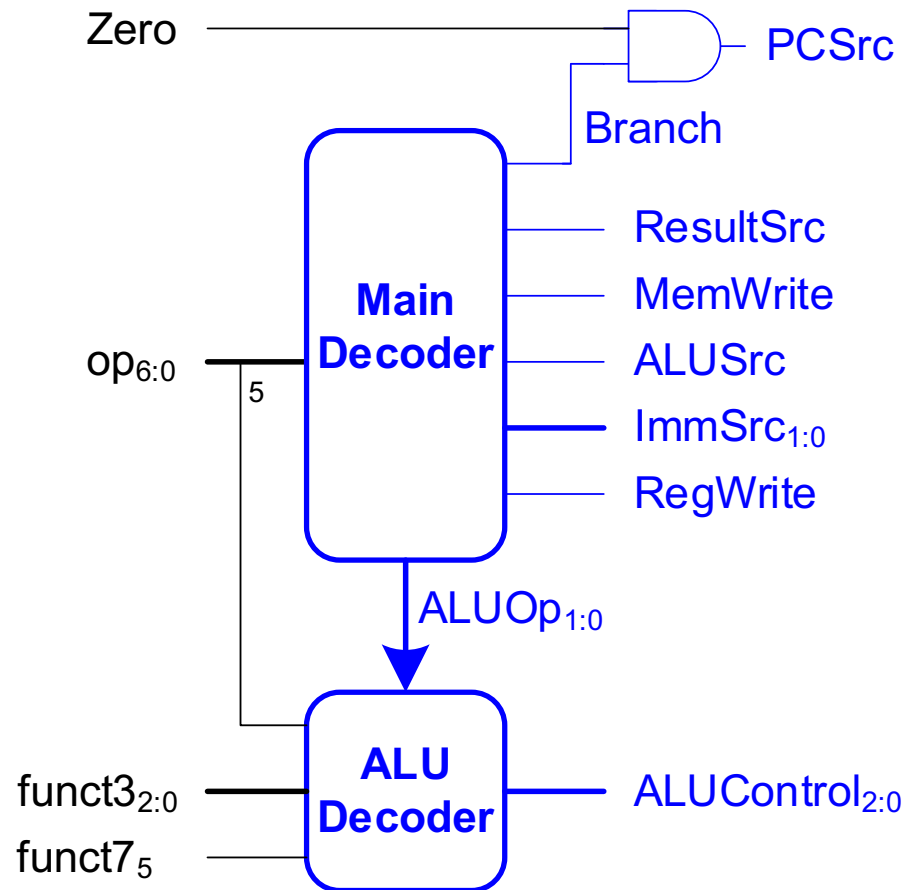


Single-Cycle Control: Main Decoder

op	Instr.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	lw							
35	sw							
51	R-type							
99	beq							

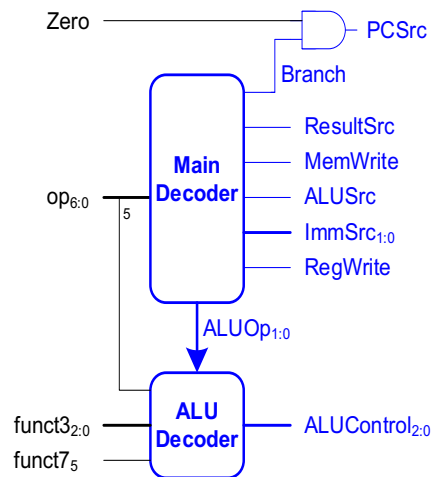


Review: ALU

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

 


Single-Cycle Control: ALU Decoder

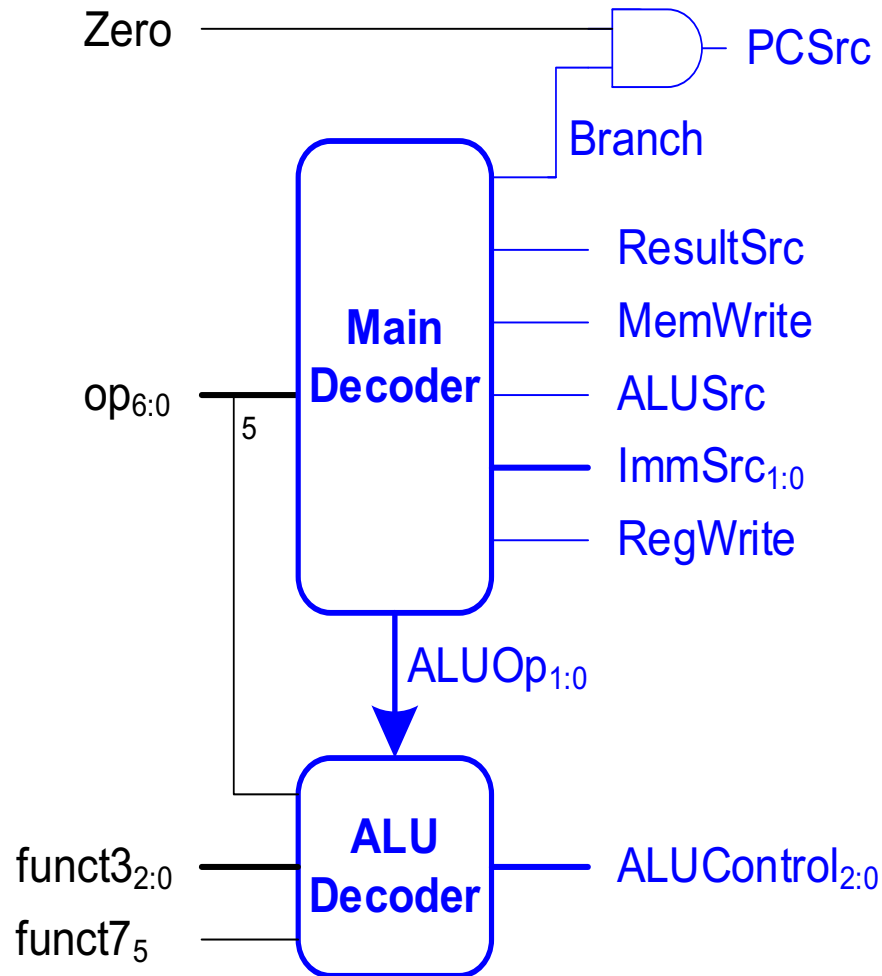


Single-Cycle Control: ALU Decoder

<i>ALUOp</i>	<i>funct3</i>	<i>op₅</i> , <i>funct7₅</i>	Instruction	<i>ALUControl_{2:0}</i>
00	x	x	lw, sw	000 (add)
01	x	x	beq	001 (subtract)
10	000	00, 01, 10	add	000 (add)
	000	11	sub	001 (subtract)
	010	x	slt	101 (set less than)
	110	x	or	011 (or)
	111	x	and	010 (and)

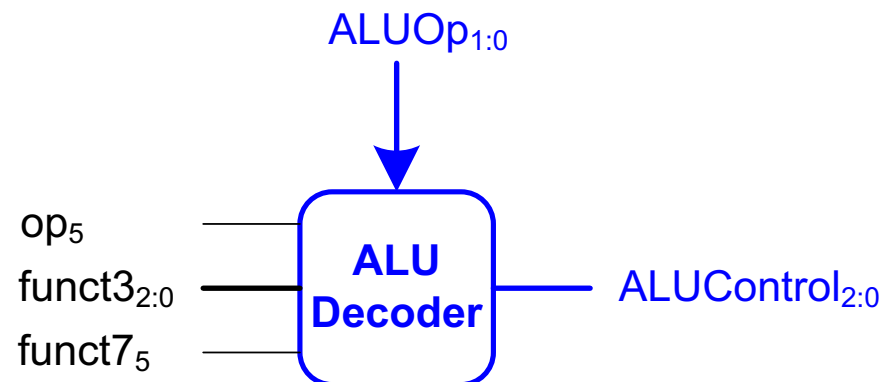

Example: and

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
51	R-type	1	XX	0	0	0	0	10

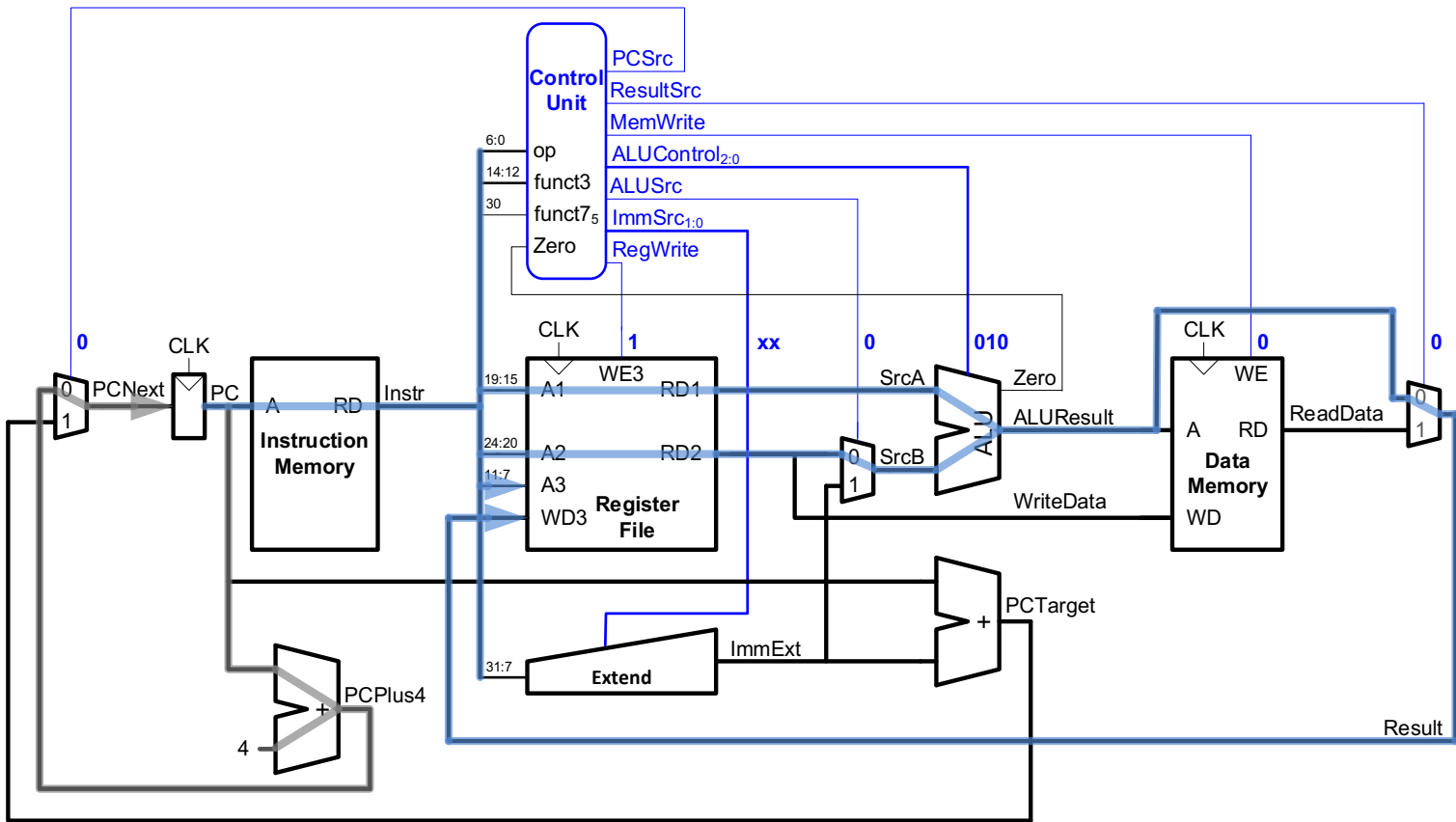


and x5, x6, x7

Chapter 7: Microarchitecture

Extending the Single-Cycle Processor

Extended Functionality: addi

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
19	I-type	1	00	1	0	0	0	10

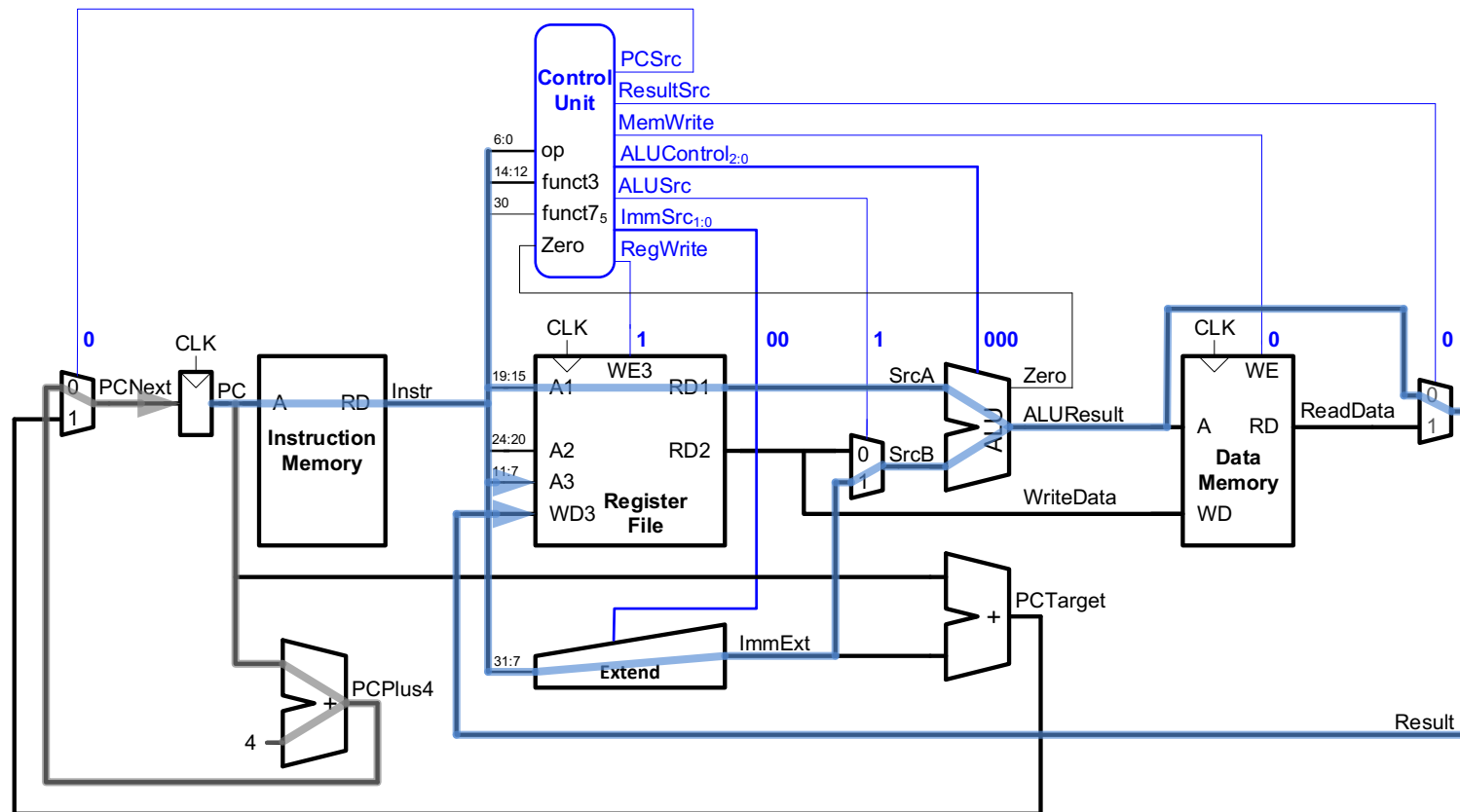

addi x5, x6, -33

Extended Functionality: I-Type ALU


op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	lw	1	00	1	0	1	0	00
35	sw	0	01	1	1	X	0	00
51	R-type	1	XX	0	0	0	0	10
99	beq	0	10	0	0	X	1	01
19	I-type	1	00	1	0	0	0	10

Extended Functionality: `jal`

Enhance the single-cycle processor to handle `jal`


- **Similar to `beq`**
- But jump is **always taken**
 - *PCSrc* should be 1
- **Immediate format** is different
 - Need a new *ImmSrc* of 11
- And `jal` must **compute $PC+4$** and **store in `rd`**
 - Take $PC+4$ from adder through ResultMux

Extended Functionality: jal

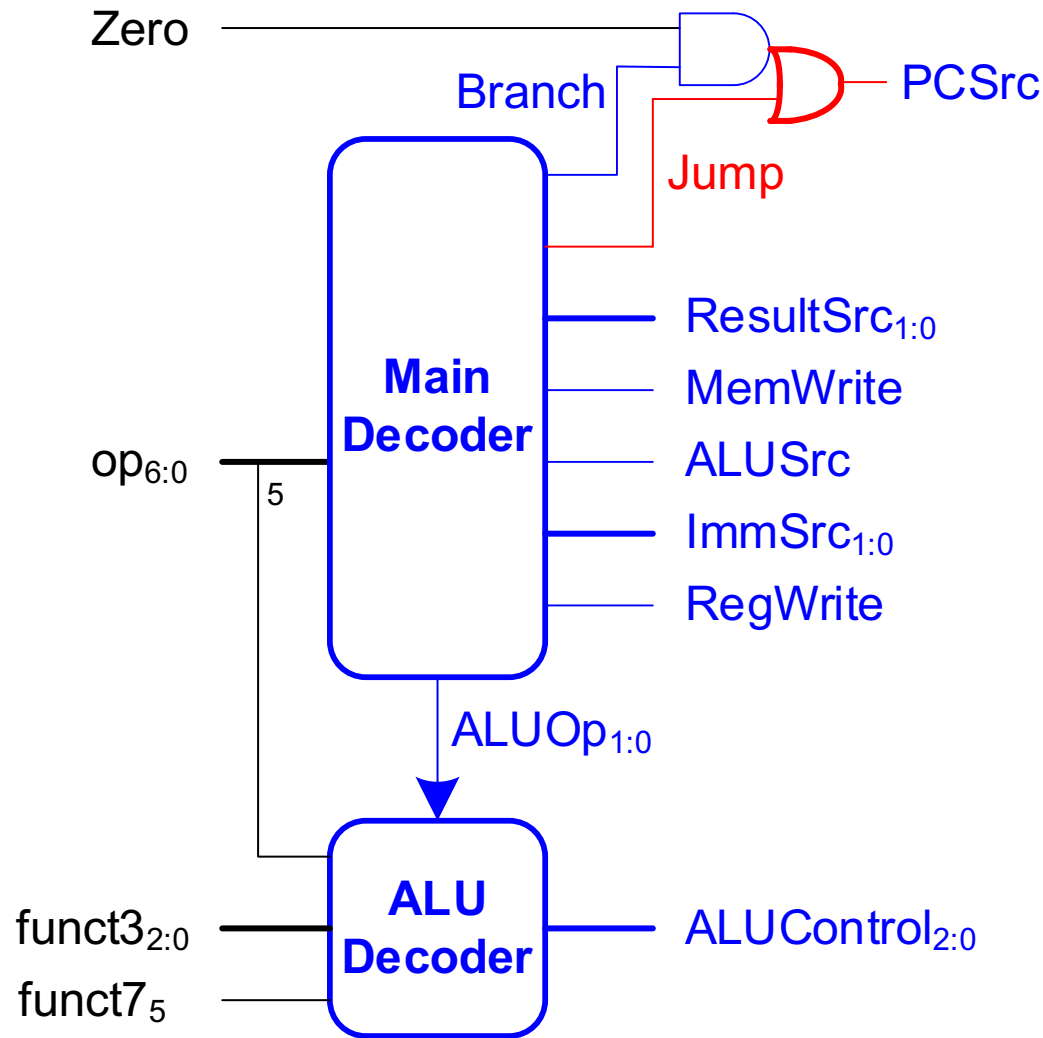

Extended Functionality: jal

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
111	jal	1	11	X	0	10	0	XX	1

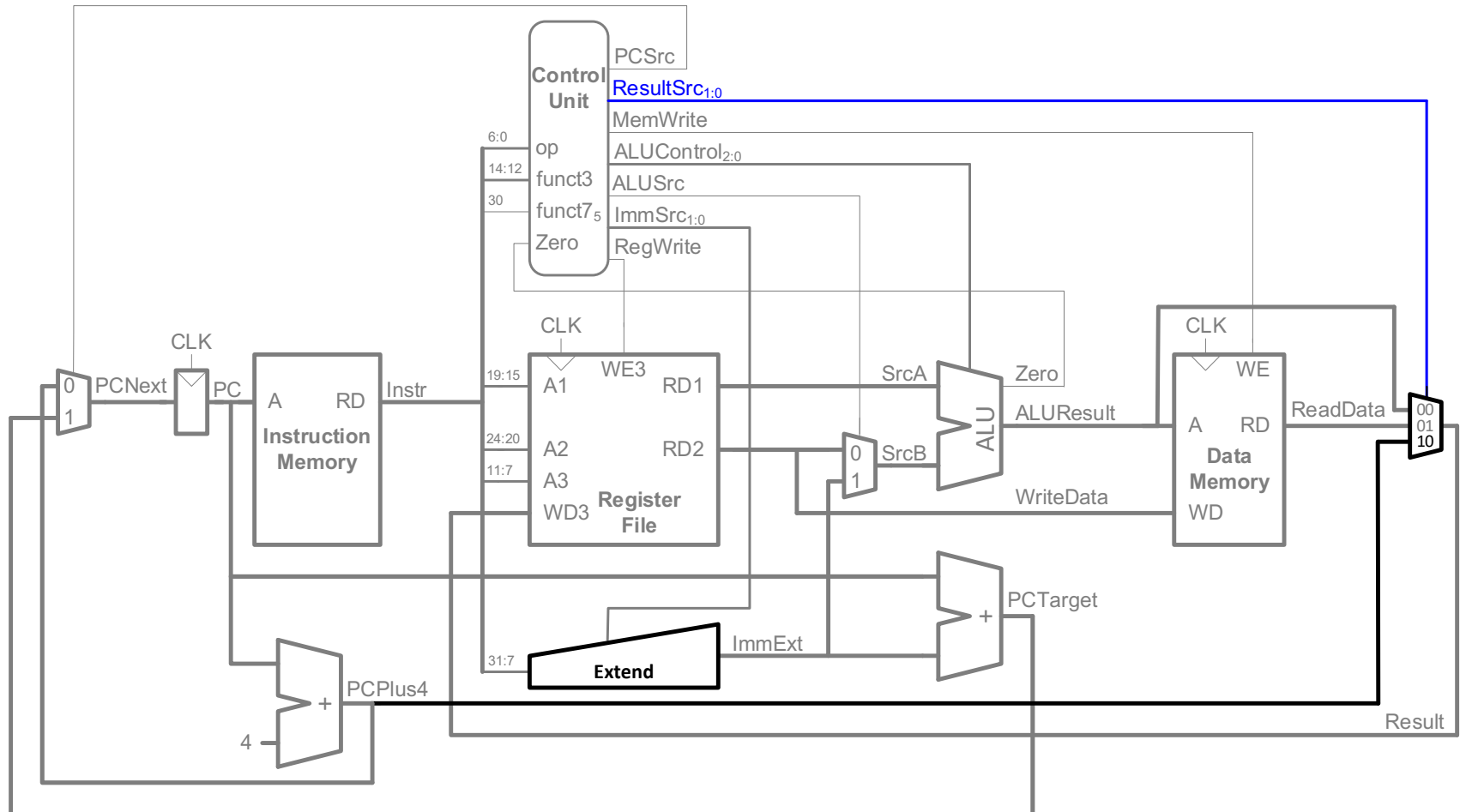


Extended Functionality: jal

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
3	lw	1	00	1	0	01	0	00	0
35	sw	0	01	1	1	XX	0	00	0
51	R-type	1	XX	0	0	00	0	10	0
99	beq	0	10	0	0	XX	1	01	0
19	l-type	1	00	1	0	00	0	10	0
111	jal	1	11	X	0	10	0	XX	1


Extended Functionality: *ImmExt*

ImmSrc _{1:0}	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20]}	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7]}	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0}	B-Type
11	{{12{instr[31]}}, instr[19:12], instr[20], instr[30:21], 1'b0}	J-Type


I-Type

 

B-Type

 

S-Type

 

J-Type



Chapter 7: Microarchitecture


Pipelined RISC-V Processor

Pipelined RISC-V Processor


- **Temporal parallelism**
- Divide single-cycle processor into **5 stages**:
 - Fetch
 - Decode
 - Execute
 - Memory
 - Writeback
- Add **pipeline registers** between stages

Single-Cycle vs. Pipelined Processor


Single-Cycle

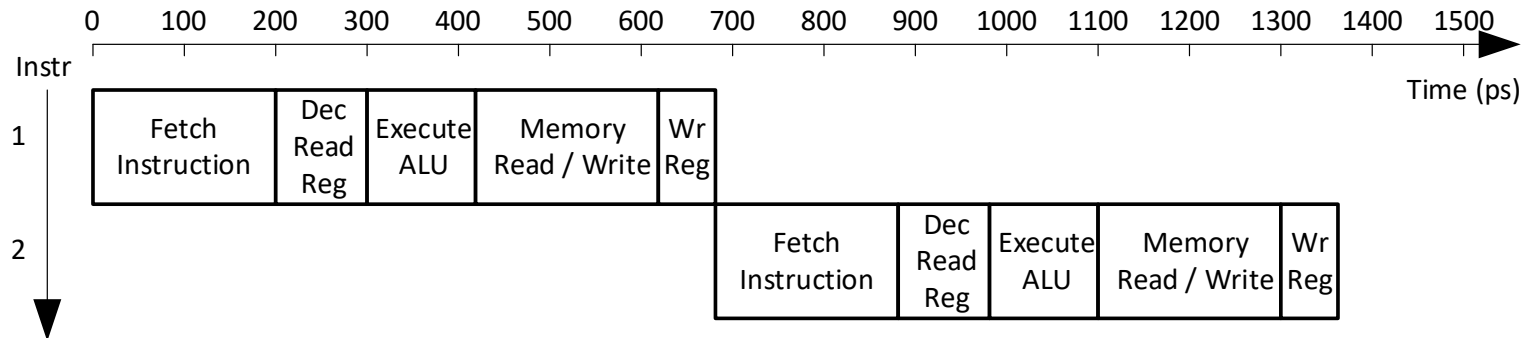



Pipelined

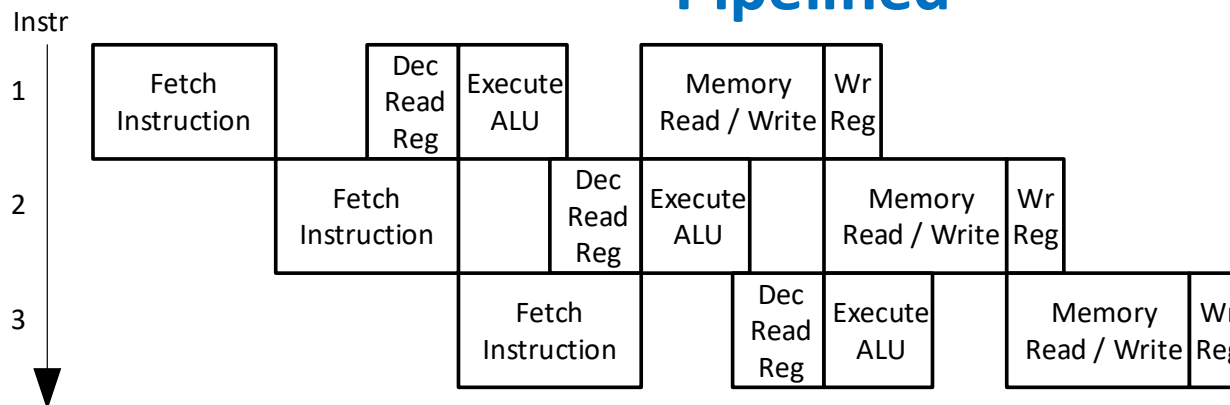

Pipelined Processor Abstraction

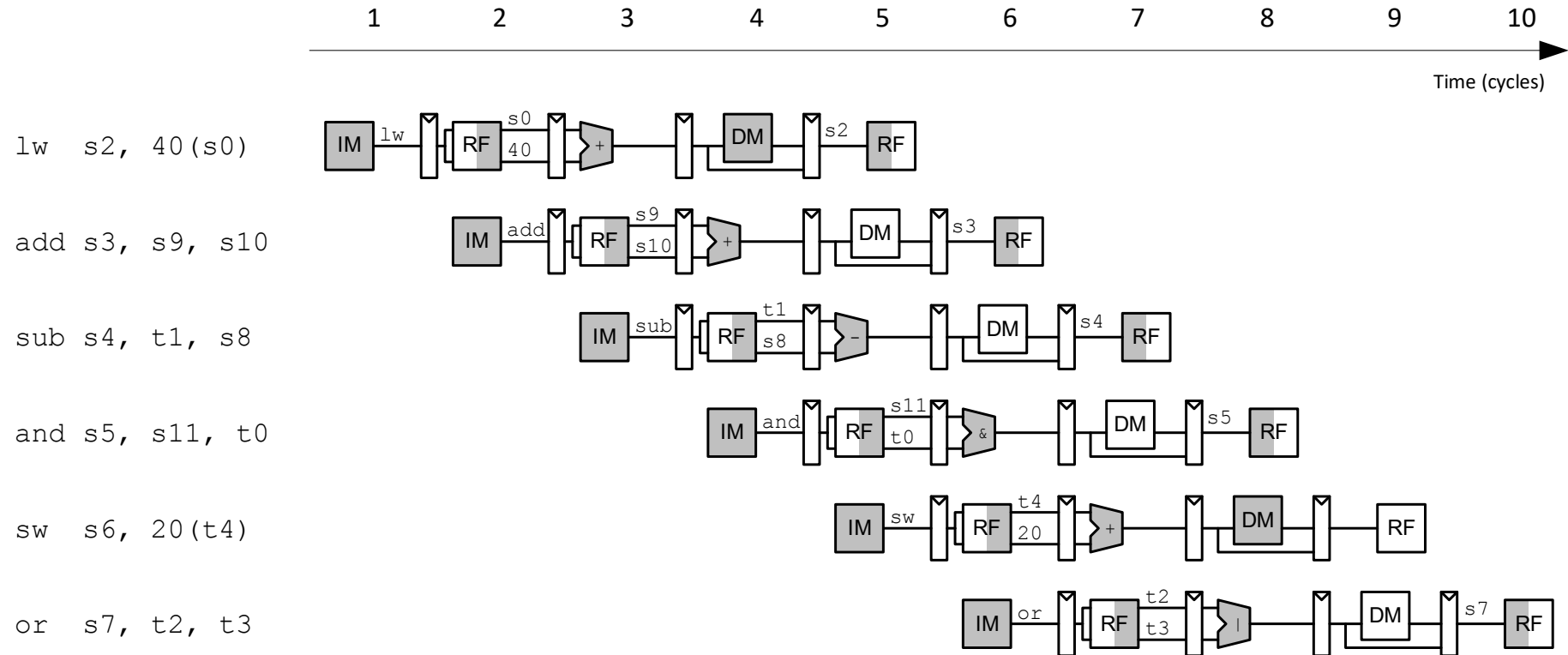


Single-Cycle & Pipelined Datapaths

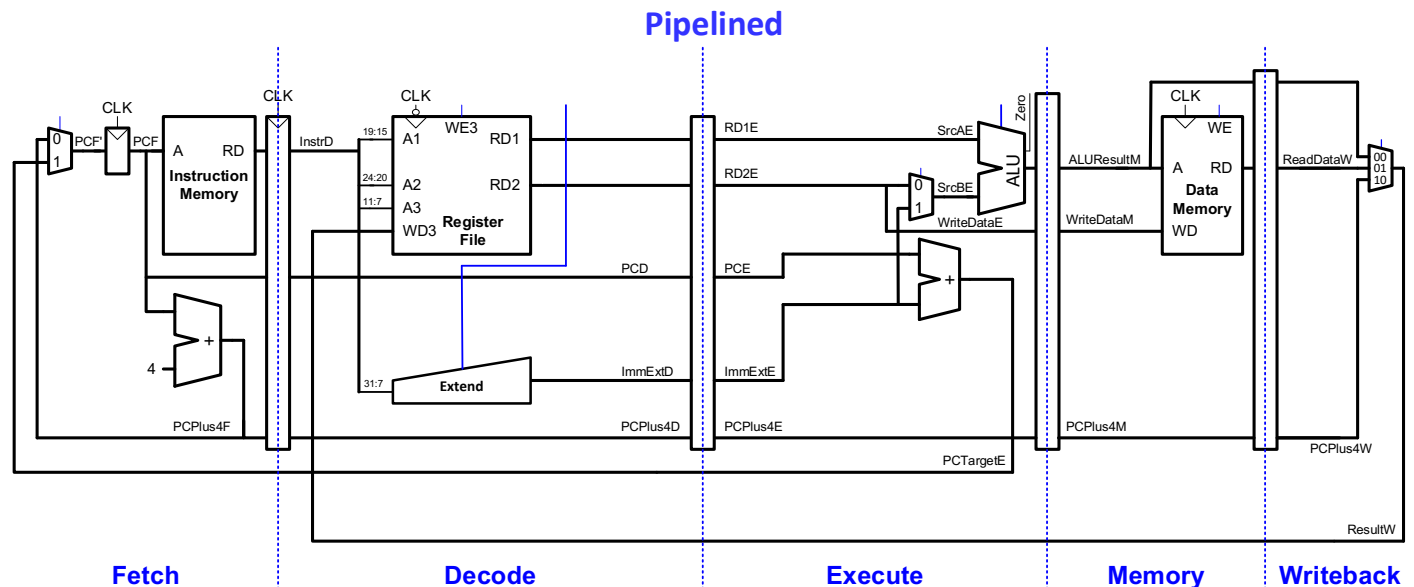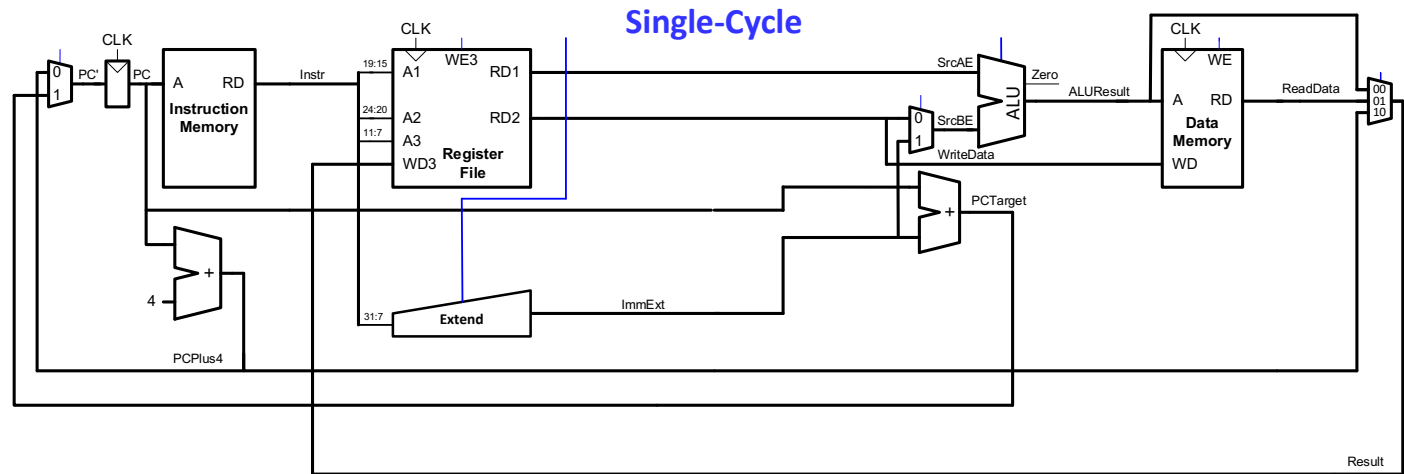


Signals in Pipelined Processor are appended with first letter of stage (i.e., PC**F**, PC**D**, PC**E**).

Corrected Pipelined Datapath

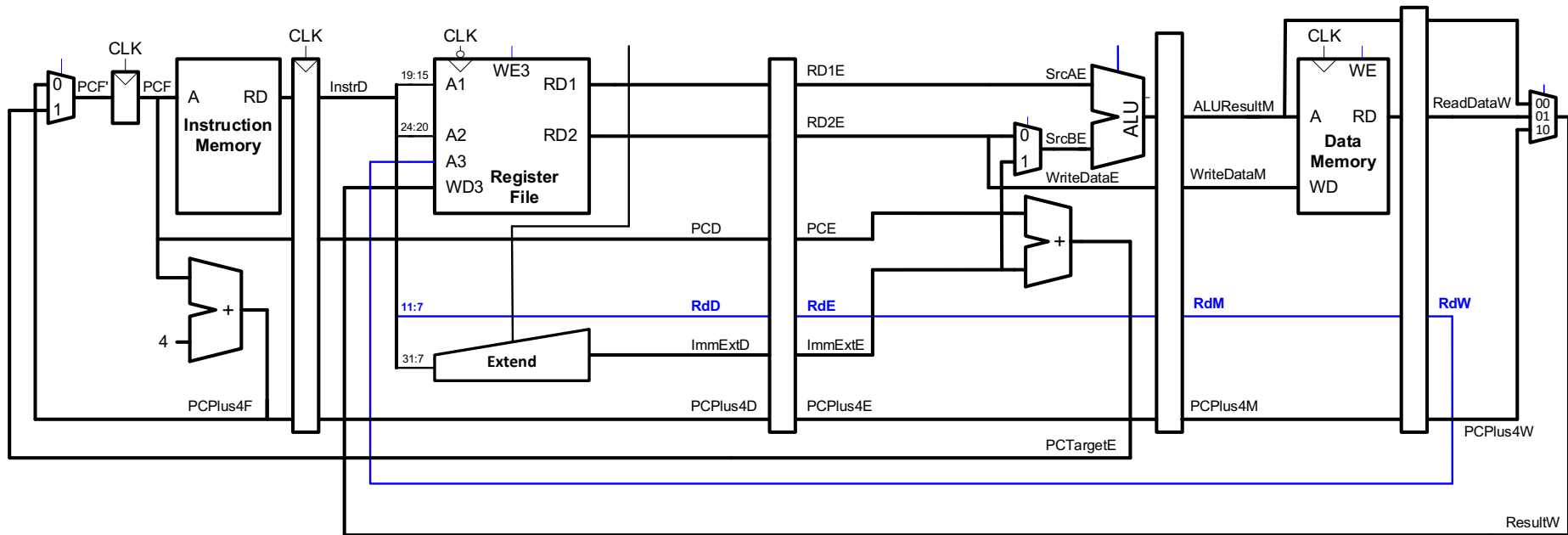

- ***Rd*** must arrive at same time as ***Result***
- Register file written on **falling edge** of *CLK*

Pipelined Processor with Control

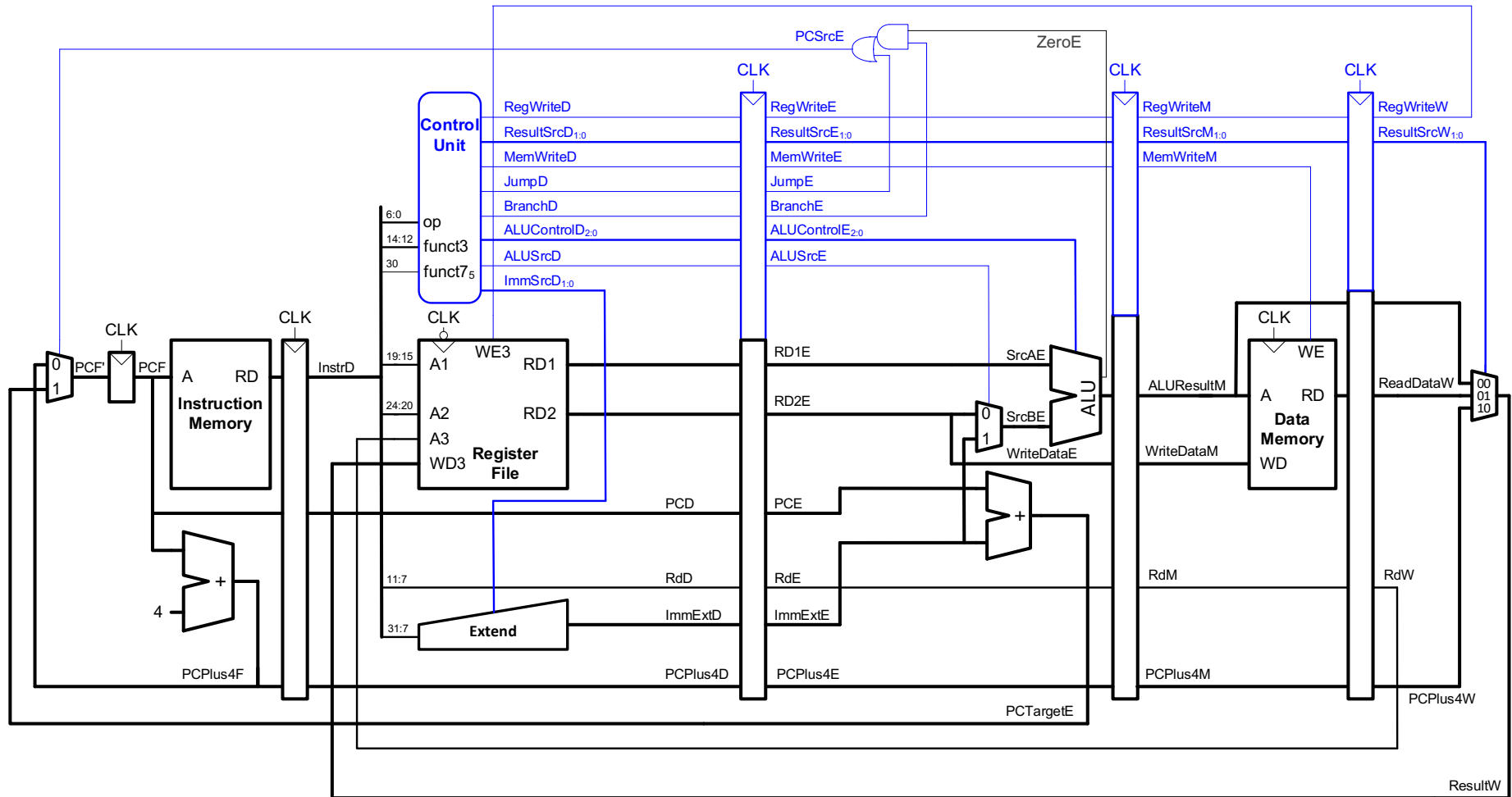

- **Same control unit** as single-cycle processor
- **Control signals travel with** the instruction (drop off when used)

Chapter 7: Microarchitecture


Pipelined Processor Hazards

Pipelined Hazards


- When an instruction depends on result from instruction that hasn't completed
- Types:
 - **Data hazard:** register value not yet written back to register file
 - **Control hazard:** next instruction not decided yet (caused by branch)

Data Forwarding

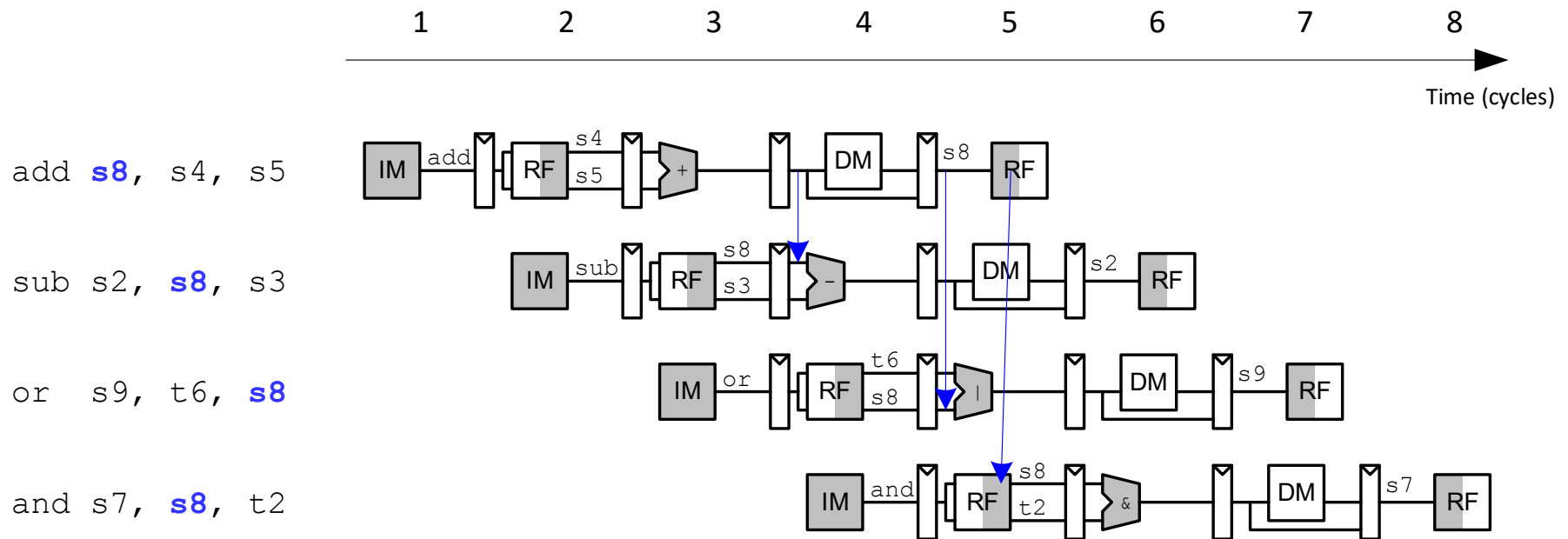- Check if source register **in Execute stage matches** destination register of instruction **in Memory or Writeback stage**.
- If so, forward result.



Data Forwarding: Hazard Unit

 

Data Forwarding

- **Case 1:** **Execute** stage $Rs1$ or $Rs2$ matches **Memory** stage Rd ?
Forward from Memory stage
- **Case 2:** **Execute** stage $Rs1$ or $Rs2$ matches **Writeback** stage Rd ?
Forward from Writeback stage
- **Case 3:** Otherwise use value read from register file (as usual)

Equations for $Rs1$:

```
if      (( $Rs1E == RdM$ ) AND  $RegWriteM$ )           // Case 1
         $ForwardAE = 10$ 
else if (( $Rs1E == RdW$ ) AND  $RegWriteW$ )           // Case 2
         $ForwardAE = 01$ 
else     $ForwardAE = 00$                            // Case 3
```

***ForwardBE** equations are similar (replace $Rs1E$ with $Rs2E$)*

Data Forwarding


- **Case 1:** **Execute** stage $Rs1$ or $Rs2$ matches **Memory** stage Rd ?
Forward from Memory stage
- **Case 2:** **Execute** stage $Rs1$ or $Rs2$ matches **Writeback** stage Rd ?
Forward from Writeback stage
- **Case 3:** Otherwise use value read from register file (as usual)

Equations for $Rs1$:


```
if      (( $Rs1E == RdM$ ) AND  $RegWriteM$ ) AND ( $Rs1E != 0$ ) // Case 1
        ForwardAE = 10
else if (( $Rs1E == RdW$ ) AND  $RegWriteW$ ) AND ( $Rs1E != 0$ ) // Case 2
        ForwardAE = 01
else    ForwardAE = 00                                     // Case 3
```

ForwardBE equations are similar (replace $Rs1E$ with $Rs2E$)

Data Hazard due to lw Dependency

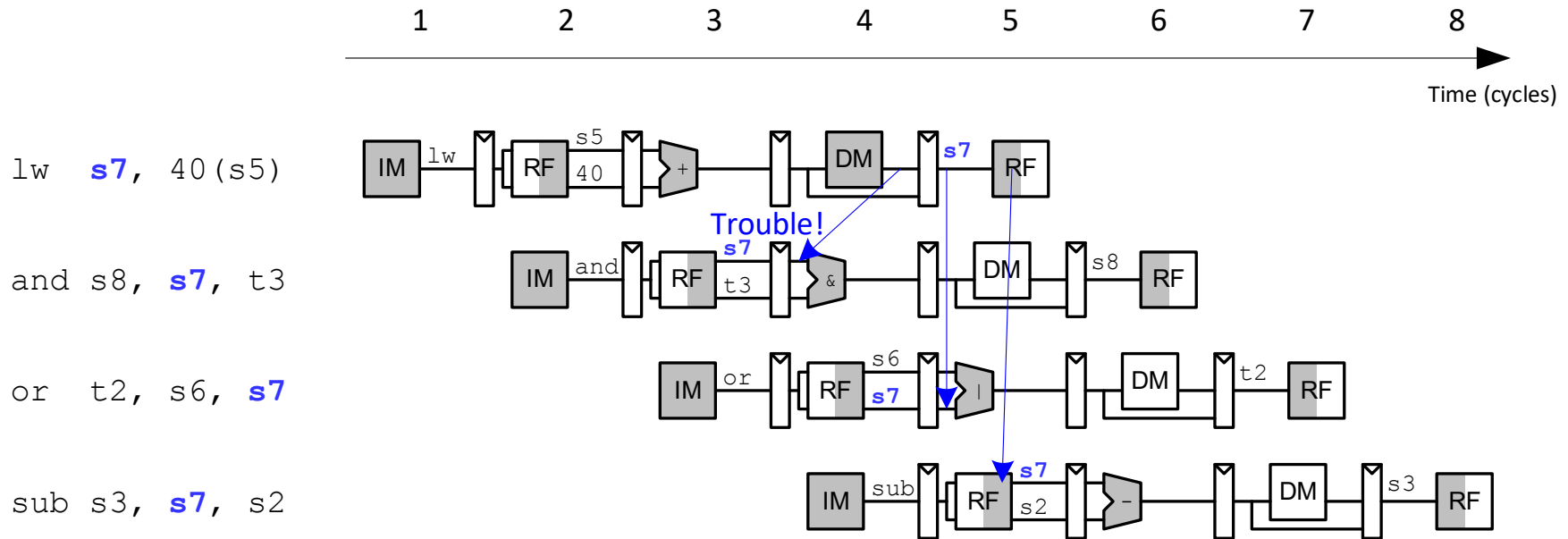

Stalling to solve 1w Data Dependency

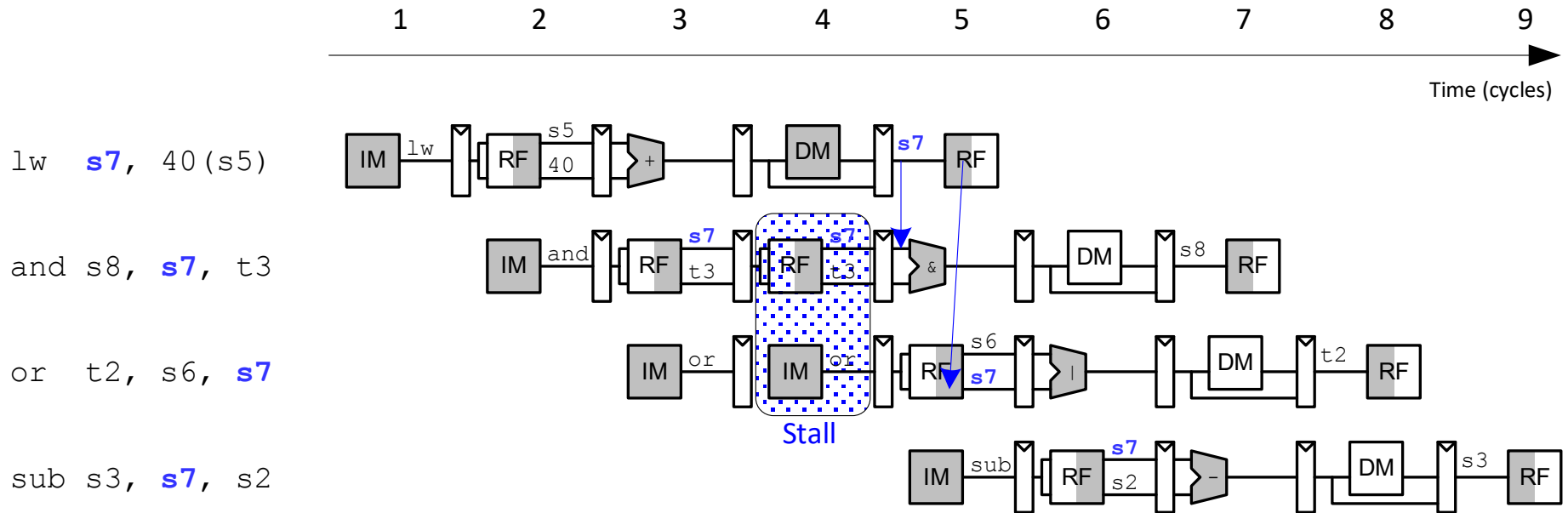

Stalling Logic

- Is either **source register in the Decode stage** the same as the **destination register in the Execute stage**?

AND


- Is the instruction in the **Execute stage a lw**?

$lwStall = ((Rs1D == RdE) \text{ OR } (Rs2D == RdE)) \text{ AND } ResultSrcE_0$

$StallF = StallD = FlushE = lwStall$

(Stall the Fetch and Decode stages, and flush the Execute stage.)

Stalling Hardware

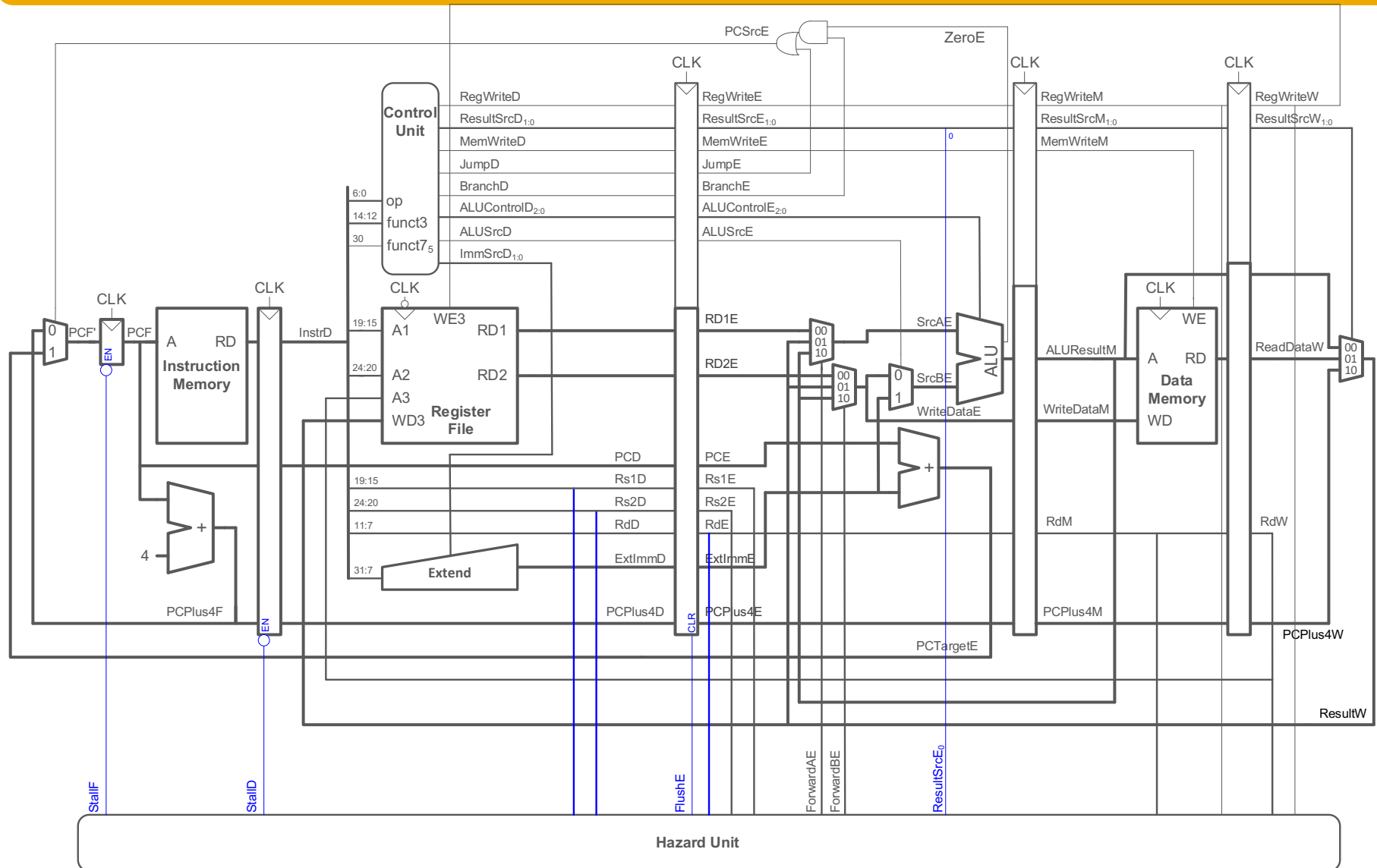


Chapter 7: Microarchitecture

Pipelined Processor Control Hazards

Control Hazards

- **beq:**
 - Branch **not determined** until the **Execute stage** of pipeline
 - **Instructions** after branch **fetch**ed before branch occurs
 - These **2 instructions must be flushed** if branch happens

Control Hazards

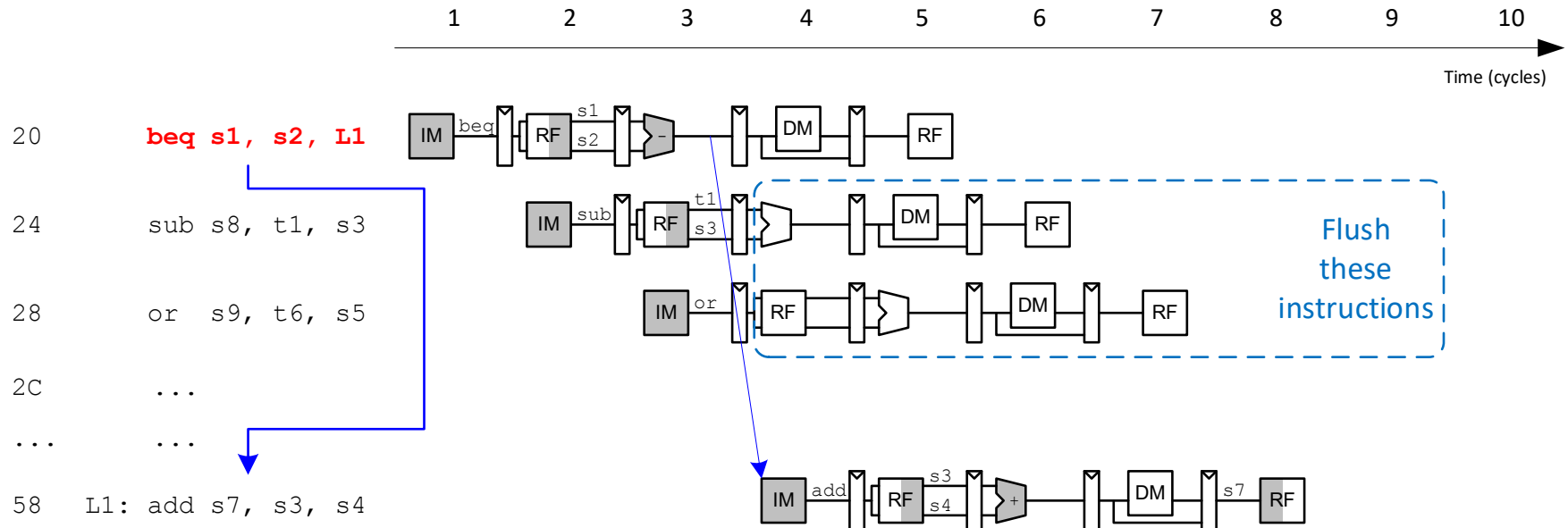

Branch misprediction penalty:

The number of instructions flushed when a branch is taken (in this case, 2 instructions)


Control Hazards: Flushing Logic

- If branch is taken in execute stage, need to flush the instructions in the Fetch and Decode stages
 - Do this by clearing Decode and Execute Pipeline registers using *FlushD* and *FlushE*
- **Equations:**


$$FlushD = PCSrcE$$

$$FlushE = lwStall \text{ OR } PCSrcE$$

Control Hazards: Flushing Hardware

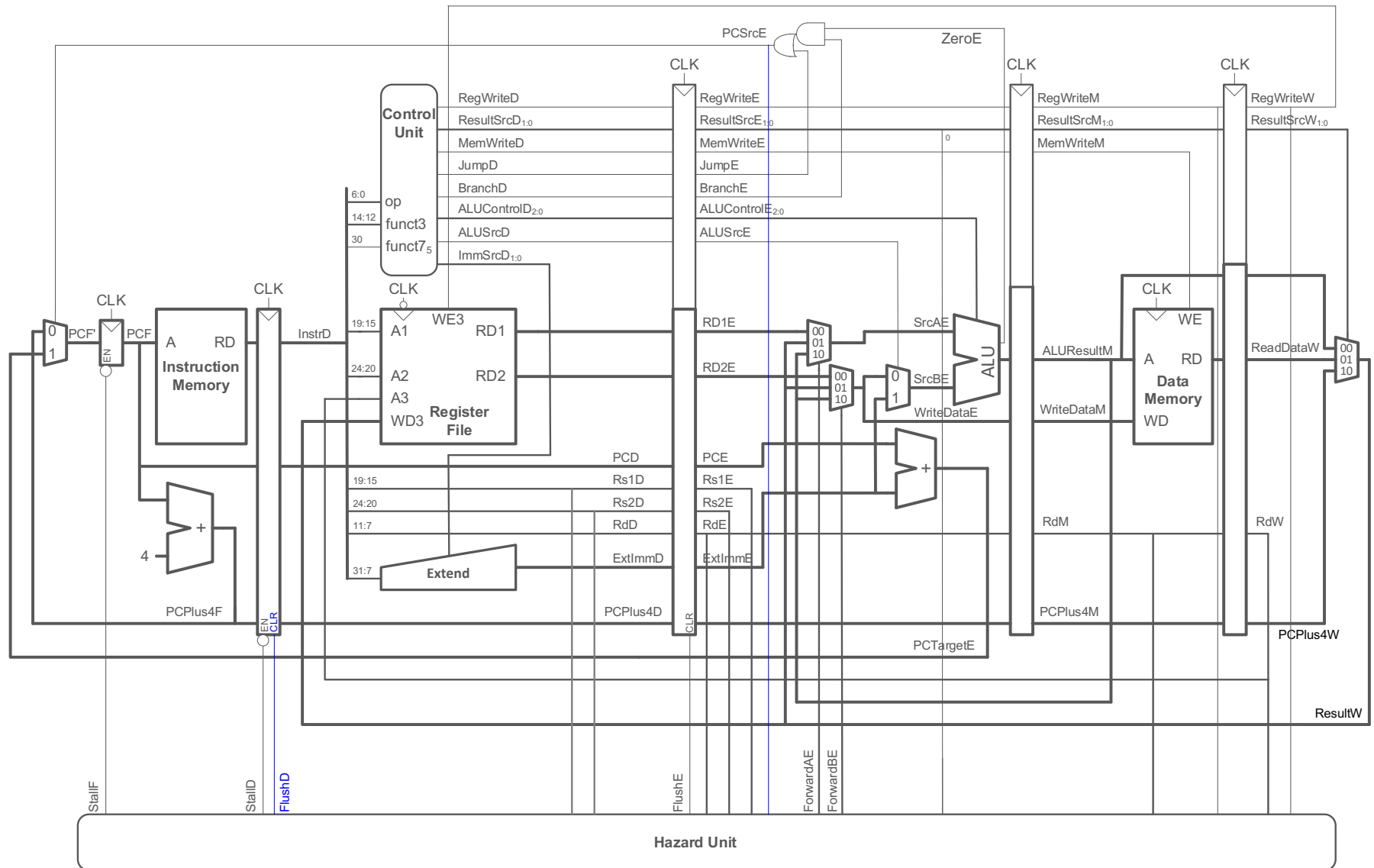

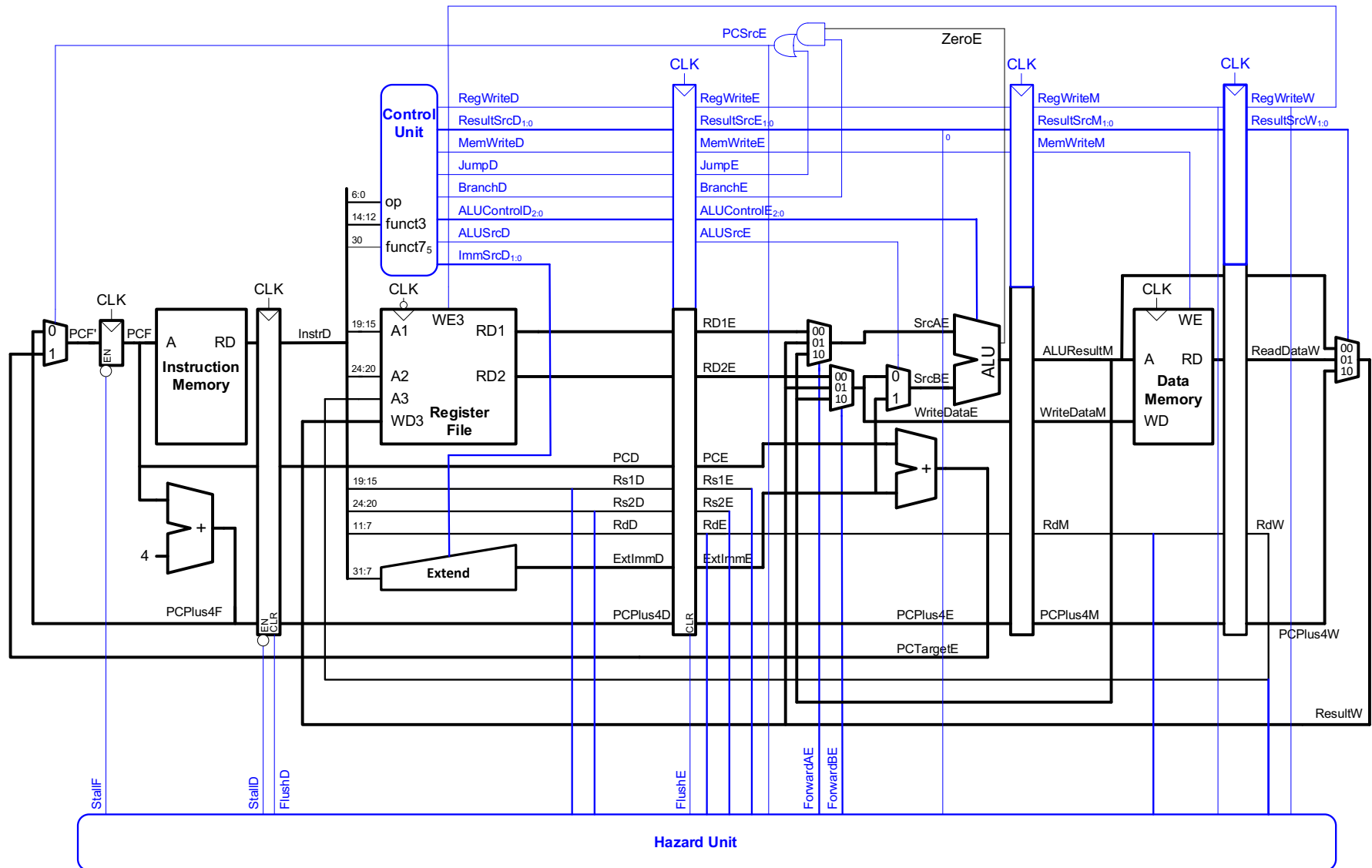RISC-V Pipelined Processor with Hazard Unit



Summary of Hazard Logic

Data hazard logic (shown for SrcA of ALU):

```
if      ((Rs1E == RdM) AND RegWriteM) AND (Rs1E != 0)    // Case 1
        ForwardAE = 10
else if ((Rs1E == RdW) AND RegWriteW) AND (Rs1E != 0)    // Case 2
        ForwardAE = 01
else      ForwardAE = 00                                // Case 3
```

Load word stall logic:

```
lwStall = ((Rs1D == RdE) OR (Rs2D == RdE)) AND ResultSrcE0
StallF = StallD = lwStall
```

Control hazard flush:

```
FlushD = PCSrcE
FlushE = lwStall OR PCSrcE
```